

Question Paper Code : 6487

B.C.A. (Semester-II) Examination, 2018

DIGITAL ELECTRONICS & COMPUTER ORGANIZATION

[BCA-S-107]

Time : Three Hours]

[Maximum Marks : 100

Note : Answer **five** questions in all. Question **No.1** is **compulsory**. Besides this, **one** question is to be attempted from each Unit.

1. Write short answers of the following : [4x10=40]
- (a) Define LATCH and its working in detail.
 - (b) Discuss the function of BUFFER.
 - (c) Differentiate between Up Counter and Down Counter.
 - (d) Define Synchronous DRAM in detail.
 - (e) Define "WORM" in terms of Computer memory.
 - (f) Prove $X+X=X$ in boolean Algebra ?
 - (g) Define Hit ratio in detail.

6487/900

(1)

[P.T.O.]

- (h) Describe Content addressable memory (CAM) in detail.
- (i) Discuss the advantages of semiconductor memory.
- (j) Define address space in detail.

UNIT-I

2. (a) Explain Exclusive gates in detail with their logic diagram and truth table. [8]
- (b) State and prove Universal property of NAND gate with appropriate diagram ? [7]
3. (a) Discuss the utility of SOP and POS techniques in circuit designing. [8]
- (b) Explain the different kinds of Magnetic Memory in detail. [7]

UNIT-II

4. Draw the K-Map and Simplify the Boolean expressions given below : [15]

$$F(ABCD) = \sum(0,2,3,4,5,6,7,12,13,14,15)$$

$$F(ABCD) = \pi(2,3,4,5,10,11,12,13,14,15)$$

6487/900

(2)

5. Design 8x1 multiplexer and explain its functioning in detail. [15]

UNIT-III

6. (a) Design the boolean logic circuit for half Subtractor and explain its functioning in detail. [8]
- (b) How flip-flops are different from Registers ? Discuss the role of Parallel load in shift register ? [7]
7. Discuss 4 bit Bidirectional shift register in detail with suitable diagram. [15]

UNIT-IV

8. (a) Explain the functioning of Master-Slave JK flip-flop with neat diagram. [8]
- (b) Discuss the utility of Encoder in detail ? [7]
9. Write short notes on the following : [5x3=15]
- (a) Associative Memory
- (b) T flip-flop
- (c) CD-ROM

----- x -----

6487/900

(3)